

# Telangana State Council Higher Education

## Notations :

- 1.Options shown in green color and with ✓ icon are correct.
- 2.Options shown in red color and with ✗ icon are incorrect.

<b>Question Paper Name :</b>	Electronics and Communication Engineering 12th Aug 2021 Shift 1
<b>Subject Name :</b>	Electronics and Communication Engineering
<b>Creation Date :</b>	2021-08-12 13:31:18
<b>Duration :</b>	120
<b>Total Marks :</b>	120
<b>Display Marks:</b>	Yes
<b>Calculator :</b>	None
<b>Magnifying Glass Required? :</b>	No
<b>Ruler Required? :</b>	No
<b>Eraser Required? :</b>	No
<b>Scratch Pad Required? :</b>	No
<b>Rough Sketch/Notepad Required? :</b>	No
<b>Protractor Required? :</b>	No
<b>Show Watermark on Console? :</b>	Yes
<b>Highlighter :</b>	No
<b>Auto Save on Console? :</b>	Yes

## Electronics and Communication Engineering

<b>Group Number :</b>	1
<b>Group Id :</b>	63643124
<b>Group Maximum Duration :</b>	0
<b>Group Minimum Duration :</b>	120

Show Attended Group? :	No
Edit Attended Group? :	No
Break time :	0
Group Marks :	120
Is this Group for Examiner? :	No

## Mathematics

Section Id :	63643144
Section Number :	1
Section type :	Online
Mandatory or Optional :	Mandatory
Number of Questions :	10
Number of Questions to be attempted :	10
Section Marks :	10
Enable Mark as Answered Mark for Review and Clear Response :	Yes
Sub-Section Number :	1
Sub-Section Id :	63643144
Question Shuffling Allowed :	Yes

Question Number : 1 Question Id : 6364312761 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical  
Correct Marks : 1 Wrong Marks : 0

If  $2x - y + z = 0$ ,  $4x - 2y + 2z = 0$  and  $6x - 3y + 3z = 0$ , then  $(x, y, z) =$

Options :

1. ✓  $(1, 2, 0)$

2. ✗  $(1, 1, -1)$

3. ✘ (0, 1, 1)

4. ✘ (3, 2, -4)

**Question Number : 2 Question Id : 6364312762 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

Which of the following is a repeated Eigen value of the matrix  $\begin{bmatrix} -1 & 2 & 2 \\ 2 & -1 & 2 \\ 2 & 2 & -1 \end{bmatrix}$

**Options :**

1. ✘ 3

2. ✔ -3

3. ✘ 4

4. ✘ -4

**Question Number : 3 Question Id : 6364312763 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

$$\int_{|z|=2} \frac{\sin z}{z^5} dz =$$

Options :

1. ✓ 0

2. ✗  $\pi i$

3. ✗  $-\pi i$

4. ✗  $2\pi i$

Question Number : 4 Question Id : 6364312764 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

$$\text{If } z = \cos^2(x + y) + \sin^2(x - y), \text{ then } \frac{\partial^2 z}{\partial x^2} - \frac{\partial^2 z}{\partial y^2} =$$

Options :

1. ✗  $\frac{\partial^2 z}{\partial x \partial y}$

$$2 \frac{\partial^2 z}{\partial x \partial y}$$

2. ✘

$$3 \frac{\partial^2 z}{\partial x \partial y}$$

3. ✘

$$0$$

4. ✔

Question Number : 5 Question Id : 6364312765 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

If C is the curve  $x^2 + y^2 = 1$ , then  $\int_C (x^2 + 3xy^2) dx + (3x^2y + y^4) dy =$

Options :

1. ✘  $2\pi$

2. ✘  $\pi$

3. ✘  $\frac{\pi}{2}$

4. ✔  $0$

Question Number : 6 Question Id : 6364312766 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The particular integral of  $y'' + 4y = x \cos x$  is  $a \sin x + b x \cos x$ , where  $(a, b) =$

Options :

1. ✘  $\left(\frac{1}{3}, \frac{2}{9}\right)$

2. ✔  $\left(\frac{2}{9}, \frac{1}{3}\right)$

3. ✘  $\left(\frac{-2}{9}, \frac{1}{3}\right)$

4. ✘  $\left(\frac{2}{3}, \frac{1}{9}\right)$

Question Number : 7 Question Id : 6364312767 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The solution of  $y'' + y = xe^x$  satisfying  $y(0) = 0$  and  $y'(0) = 1$  is  $y = k(\cos x + 2\sin x)$ , where  $k =$

Options :

1. ✘ 1

2. ✘  $\frac{1}{3}$

3. ✔  $\frac{1}{2}$

4. ✘  $\frac{1}{4}$

**Question Number : 8 Question Id : 6364312768 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

In a normal distribution, the ratio between quartile deviation, mean deviation and standard deviation is

**Options :**

1. ✘ 3 : 4 : 5

2. ✘ 7 : 8 : 10

3. ✔ 10 : 12 : 15

4. ✘ 8 : 12 : 15

Question Number : 9 Question Id : 6364312769 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

A variate X has the probability distribution

x	-1	0	1	2
P(X = x)	$\frac{1}{3}$	$\frac{1}{4}$	$\frac{1}{6}$	$\frac{3}{4}$

Then E(X) =

Options :

1. ✘ 4
2. ✘  $\frac{8}{7}$
3. ✔  $\frac{4}{3}$
4. ✘  $\frac{8}{3}$

Question Number : 10 Question Id : 6364312770 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0



The largest positive root of the equation  $x^3 - 5x^2 + 6x - 1 = 0$  lies in the interval

Options :

1. ✘ (2, 3)
2. ✔ (3, 4)
3. ✘ (4, 5)
4. ✘ (5, 6)

## Electronics and Communication Engineering

Section Id :	63643145
Section Number :	2
Section type :	Online
Mandatory or Optional :	Mandatory
Number of Questions :	110
Number of Questions to be attempted :	110
Section Marks :	110
Enable Mark as Answered Mark for Review and Clear Response :	Yes
Sub-Section Number :	1
Sub-Section Id :	63643145
Question Shuffling Allowed :	Yes

Question Number : 11 Question Id : 6364312771 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The unit of  $\frac{R}{2} \sqrt{\frac{L}{C}}$  is

Options :

1. ✘ No unit
2. ✘  $\Omega$
3. ✘  $\Omega$ H rad
4. ✔  $\Omega^2$

Question Number : 12 Question Id : 6364312772 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is  
Question Mandatory : No Option Orientation : Vertical  
Correct Marks : 1 Wrong Marks : 0

The initial value of  $z(t)$ ,  $z(s) = \frac{s^2+3}{s^3+4s^2+6}$  is

Options :

1. ✘ s
2. ✔ 1
3. ✘ 0

4. ✘  $s^2$

**Question Number : 13 Question Id : 6364312773 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

For a two port reciprocal bilateral network the transmission parameters are

$A = 1, B = 5,$  and  $D = 1,$  the parameter  $C$  will be

**Options :**

1. ✘ 0.8

2. ✔ 1.4

3. ✘ 0.7

4. ✘ 1.2

**Question Number : 14 Question Id : 6364312774 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

A typical two port network is characterized by  $2V_1 + 4V_2 = I_1$  and

$6V_1 + V_2 = 8I_2.$  The value of  $h_{21}$  is

**Options :**

1. ✘ 0.235

2. ✘ 0.325

3. ✔ 0.375

4. ✘ 0.525

**Question Number : 15 Question Id : 6364312775 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

When determining Thevenin's resistance of a circuit

Options :

1. ✘ All sources must be open circuited

2. ✘ All sources must be short circuited

3. ✘ All voltage sources must be open circuited and all current sources must be short circuited

4. ✔ All sources must be replaced by their internal resistances

**Question Number : 16 Question Id : 6364312776 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

Three resistance of  $15\Omega$  each are connected in delta. The resistance of equivalent star will have a value of

Options :

1. ✘  $12\Omega$
2. ✔  $5\Omega$
3. ✘  $5/3\Omega$
4. ✘  $45\Omega$

Question Number : 17 Question Id : 6364312777 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

If a two-port network is reciprocal, then the usual relationship is

Options :

1. ✔  $h_{12} = -h_{21}$
2. ✘  $h_{12} = h_{21}$
3. ✘  $h_{11} = h_{22}$

4. ✘  $h_{11}h_{22} - h_{12}h_{21} = 1$

Question Number : 18 Question Id : 6364312778 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

A non-ideal voltage source  $V_s$  has an internal impedance of  $z_s$ . If a purely resistive load is to be chosen that maximizes the power transferred to the load, its values must be

Options :

1. ✔ Magnitude of  $z_s$

2. ✘ 0

3. ✘ Real part of  $z_s$

4. ✘ Complex conjugate of  $z_s$

Question Number : 19 Question Id : 6364312779 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The graph of an electrical network has N nodes and B branches. The number of links L, with respect to the choice of a tree is given by

Options :

1. ✘  $N - B + 1$

2. ✘  $B + N$

3. ✔  $B - N + 1$

4. ✘  $N - 2B - 1$

**Question Number : 20 Question Id : 6364312780 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

A unit step voltage is applied at  $t = 0$  to a series RL circuit with zero initial conditions

**Options :**

1. ✘ It is possible for the current to be oscillatory.

2. ✔ The voltage across the resistor at  $t = 0^+$  is zero.

3. ✘ The energy stored in inductor in the steady state is zero.

4. ✘ The resistor current eventually falls to zero.

**Question Number : 21 Question Id : 6364312781 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

For a voltage source

**Options :**

1. ✘ Terminal voltage is equal to the source e.m.f.
2. ✔ Terminal voltage cannot exceed source e.m.f.
3. ✘ Terminal voltage is always lower than source e.m.f.
4. ✘ Terminal voltage is higher than source e.m.f.

**Question Number : 22 Question Id : 6364312782 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The theorem that enables a number of voltage (or current) sources to be combined directly into a single voltage (or current) source is the

**Options :**

1. ✘ Compensation theorem
2. ✘ Reciprocity theorem
3. ✔ Milliman's theorem
4. ✘ Maxwell's theorem

**Question Number : 23 Question Id : 6364312783 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**



**Correct Marks : 1 Wrong Marks : 0**

Nodal analysis is based on

**Options :**

1. ✓ KCL
2. ✗ KVL
3. ✗ KCL and KVL
4. ✗ Law of conservation of energy

**Question Number : 24 Question Id : 6364312784 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is**

**Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

A network consists only of independent current sources and resistors. If the values of all the current sources are doubled, then values of node voltages

**Options :**

1. ✗ Remains same
2. ✓ Will be doubled
3. ✗ Will be halved
4. ✗ Changes in some other way

**Question Number : 25 Question Id : 6364312785 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The type of systems which are characterized by the input and output quantized at certain levels are called as

**Options :**

1. ✓ Analog
2. ✗ Discrete
3. ✗ Continuous
4. ✗ Digital

**Question Number : 26 Question Id : 6364312786 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

An example of a discrete set of information/system is

**Options :**

1. ✗ The trajectory of the Sun
2. ✓ Data on a CD
3. ✗ Universe time scale

4. ✘ Movement of water through a pipe

Question Number : 27 Question Id : 6364312787 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

A system which is linear is said to obey the rules of

Options :

1. ✘ Scaling
2. ✘ Additivity
3. ✔ Both scaling and additivity
4. ✘ Homogeneity

Question Number : 28 Question Id : 6364312788 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

A time invariant system is a system whose output

Options :

1. ✘ Increases with a delay in input
2. ✘ Decreases with a delay in input

3. ✓ Remains same with a delay in input

4. ✗ Vanishes with a delay in input

**Question Number : 29 Question Id : 6364312789 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

All real time systems concerned with the concept of causality are

**Options :**

1. ✗ Non causal

2. ✓ Causal

3. ✗ Neither causal nor non causal

4. ✗ Memoryless

**Question Number : 30 Question Id : 6364312790 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

A system is said to be defined as non-causal, when

**Options :**

1. ✗ The output at the present depends on the input at an earlier time

2. ✘ The output at the present does not depend on the factor of time at all
3. ✘ The output at the present depends on the input at the current time
4. ✔ The output at the present depends on the input at a time instant in the future

**Question Number : 31 Question Id : 6364312791 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

If  $F(s) = L\{f(t)\} = \frac{2s+1}{s^2+4s+1}$  then the initial and final values of  $f(t)$  are respectively

**Options :**

1. ✘ 0, 2
2. ✔ 2, 0
3. ✘ 0, 2/7
4. ✘ 2/7, 0

**Question Number : 32 Question Id : 6364312792 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

A system with transfer function  $H(z)$  has impulse response  $h(.)$  defined as  $h(2) = 1$ ,  $h(3) = -1$  and  $h(k) = 0$  otherwise. Consider the following statements

$S_1$ :  $H(z)$  is a low pass filter

$S_2$ :  $H(z)$  is an FIR filter

Which of the following is correct

Options :

1. ✓ Only  $S_1$  is true
2. ✗ Both  $S_1$  and  $S_2$  are false
3. ✗ Both  $S_1$  and  $S_2$  are true and  $S_2$  is a reaction for  $S_1$
4. ✗ Both  $S_1$  and  $S_2$  are true and  $S_2$  is not a reaction for  $S_1$

Question Number : 33 Question Id : 6364312793 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The 3-dB bandwidth of the low pass signal  $e^{-t} u(t)$  where  $u(t)$  is the unit step function is given by

Options :

1. ✓  $1/2\pi$  Hz
2. ✗  $\frac{\sqrt{\sqrt{2}-1}}{2\pi}$  Hz

3. ✘ Infinity

4. ✘ 1 Hz

Question Number : 34 Question Id : 6364312794 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The Laplace transform of a continuous time signal  $x(t)$  is  $X(s) = (5-s)/s^2 - s - 2$ . If the Fourier transform of this signal exists, then  $x(t)$  is

Options :

1. ✘  $e^{2t} u(t) - 2 e^{-t} u(t)$

2. ✘  $-e^{2t} u(-t) + 2 e^{-t} u(t)$

3. ✘  $-e^{2t} u(-t) - 2 e^{-t} u(t)$

4. ✔  $e^{2t} u(-t) - 2 e^{-t} u(t)$

Question Number : 35 Question Id : 6364312795 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

If the impulse response of a discrete-time system is  $h[n] = -5^{-n} u[-n-1]$  then the system function  $H(z)$  is equal to

Options :

1. ✘  $\frac{-z}{z-5}$  and the system is stable

2. ✔  $\frac{z}{z-5}$  and the system is stable

3. ✘  $\frac{-z}{z-5}$  and the system is unstable

4. ✘  $\frac{z}{z-5}$  and the system is unstable

Question Number : 36 Question Id : 6364312796 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0



The impulse response functions of four linear systems are  $S_1$ ,  $S_2$ ,  $S_3$ , and  $S_4$  are given respectively by

$$h_1(t) = 1, \quad h_2(t) = t.u(t), \quad h_3(t) = u(t)/t+1, \quad h_4(t) = e^{-3t}u(t)$$

where  $u(t)$  is the unit step function. Which of these systems is time invariant, causal and stable

Options :

1. ✘  $S_1$

2. ✘  $S_2$

3. ✘  $S_3$

4. ✔  $S_4$

Question Number : 37 Question Id : 6364312797 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The Fourier transform of a conjugate symmetric function is always

Options :

1. ✘ Imaginary

2. ✘ Conjugate anti-symmetric

3. ✓ Real

4. ✗ Conjugate symmetric

**Question Number : 38 Question Id : 6364312798 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

For a BJT the common base current gain  $\alpha = 0.98$  and the collector base junction reverse bias saturation current  $I_{CO} = 0.6\mu\text{A}$ . This BJT is connected in the common emitter mode and operated in the active region with a base drive current  $I_B = 20\mu\text{A}$ . The collector current  $I_C$  for this mode of operation is

**Options :**

1. ✗ 0.98 mA

2. ✗ 0.99 mA

3. ✗ 1.0 mA

4. ✓ 1.01 mA

**Question Number : 39 Question Id : 6364312799 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

At room temperature, a possible value for the mobility of electrons in the inversion layer of silicon n-channel MOSFET is

Options :

1. ✘ 450 cm<sup>2</sup>/V-s
2. ✔ 1350 cm<sup>2</sup>/V-s
3. ✘ 1800 cm<sup>2</sup>/V-s
4. ✘ 3600 cm<sup>2</sup>/V-s

Question Number : 40 Question Id : 6364312800 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

In a uniformly doped BJT, assume that  $N_E$ ,  $N_B$  and  $N_C$  are the emitter, base and collector dopings in atoms/cm<sup>3</sup>, respectively. If the emitter injection efficiency of the BJT is close to unity, which one of the following conditions is true

Options :

1. ✘  $N_E = N_B = N_C$
2. ✔  $N_E \geq N_B$  and  $N_B > N_C$
3. ✘  $N_E = N_B$  and  $N_B < N_C$

4. ✘  $N_E < N_B < N_C$

Question Number : 41 Question Id : 6364312801 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

Consider the following two statements about the internal conditions in an n-channel MOSFET operating in the active region

S1: The inversion charge decreases from source to drain

S2: The channel potential increases from source to drain

Options :

- 1. ✘ Only  $S_2$  is true
- 2. ✘ Both  $S_1$  and  $S_2$  false
- 3. ✘ Both  $S_1$  and  $S_2$  are true but  $S_2$  is not a reason of  $S_1$
- 4. ✔ Both  $S_1$  and  $S_2$  are true but  $S_2$  is a reason of  $S_1$

Question Number : 42 Question Id : 6364312802 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

Thin gate oxide in a CMOS process is preferably grown using

Options :

1. ✘ Wet oxidation
2. ✔ Dry oxidation
3. ✘ Epitaxial deposition
4. ✘ Ion implantation

Question Number : 43 Question Id : 6364312803 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

In an n-type silicon crystal at room temperature, which of the following can have a concentration of  $4 \times 10^{-19} \text{ cm}^{-3}$

Options :

1. ✘ Silicon atom
2. ✘ Holes
3. ✔ Dopant atoms
4. ✘ Valence electrons

Question Number : 44 Question Id : 6364312804 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

Which of the following is not associated with a p-n junction

Options :

1. ✘ Junction capacitance
2. ✘ Charge storage capacitance
3. ✘ Depletion capacitance
4. ✔ Channel length modulation

Question Number : 45 Question Id : 6364312805 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

A  $p^+n$  junction has a built-in potential of 0.8 V. The depletion layer width at a reverse bias of 1.2 V is  $2\mu\text{m}$ . For a reverse bias of 7.2 V, the depletion layer width will be

Options :

1. ✔  $4\mu\text{m}$
2. ✘  $4.9\mu\text{m}$
3. ✘  $8\mu\text{m}$

4. ✘ 12  $\mu\text{m}$

**Question Number : 46 Question Id : 6364312806 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

Under low level injection assumption, the injected minority carrier current for an extrinsic semiconductor is essentially, the

**Options :**

1. ✔ Diffusion current
2. ✘ Drift current
3. ✘ Recombination current
4. ✘ Induced current

**Question Number : 47 Question Id : 6364312807 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

A Silicon PN junction at a temperature of  $20^\circ\text{C}$  has a reverse saturation current of 10 pico-Amperes (pA). The reverse saturation current at  $40^\circ\text{C}$  for the same bias is approximately

**Options :**

1. ✘ 30 pA
2. ✔ 40 pA
3. ✘ 50 pA
4. ✘ 60 pA

Question Number : 48 Question Id : 6364312808 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The drain of an n-channel MOSFET is shorted to the gate so that  $V_{GS} = V_{DS}$ . The threshold voltage ( $V_T$ ) of MOSFET is 1V. If the drain current ( $I_D$ ) is 1mA for  $V_{GS} = 2V$ , then for  $V_{GS} = 3V$ ,  $I_D$  is

Options :

1. ✘ 2 mA
2. ✘ 3 mA
3. ✘ 9 mA
4. ✔ 4 mA

Question Number : 49 Question Id : 6364312809 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is



**Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

Consider an abrupt p-junction. Let  $V_{bi}$  be the built-in potential of this junction and  $V_R$  be the applied reverse bias. If the junction capacitance ( $C_j$ ) is 1pF for  $V_{bi} + V_R = 1V$ , then for  $V_{bi} + V_R = 4V$ ,  $C_j$  will be

**Options :**

1. ✘ 4 pF
2. ✘ 2 pF
3. ✘ 0.25 pF
4. ✔ 0.5 pF

**Question Number : 50 Question Id : 6364312810 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is**

**Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

If P is passivation, Q is n-well implant, R is metallization, and S is source/drain diffusion, then the order in which they are carried out in a standard n-well CMOS fabrication process, is

**Options :**

1. ✘ P-Q-R-S
2. ✔ Q-S-R-P

3. ✘ R-P-S-Q

4. ✘ S-R-Q-P

**Question Number : 51 Question Id : 6364312811 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The input impedance ( $Z_i$ ) and output impedance ( $Z_o$ ) of an ideal transconductance (Voltage Controlled Current Source)

**Options :**

1. ✘  $Z_i = 0, Z_o = 0$

2. ✘  $Z_i = \infty, Z_o = 0$

3. ✔  $Z_i = \infty, Z_o = \infty$

4. ✘  $Z_i = 0, Z_o = \infty$

**Question Number : 52 Question Id : 6364312812 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

As a temperature increased, the voltage across a diode carrying a constant current

**Options :**

1. ✓ Decreases
2. ✘ Increases
3. ✘ Remain constant
4. ✘ May increase or decrease depending upon the doping levels in the junction

**Question Number : 53 Question Id : 6364312813 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The use of rectifier filter in a capacitor circuit gives satisfactory performance only when load

**Options :**

1. ✘ Current is high
2. ✘ Voltage is high
3. ✓ Current is low
4. ✘ Voltage is low

Question Number : 54 Question Id : 6364312814 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is  
Question Mandatory : No Option Orientation : Vertical  
Correct Marks : 1 Wrong Marks : 0

The threshold voltage of an n-channel MOSFET can be increased by

Options :

1. ✘ Reducing gate oxide thickness
2. ✘ Increasing channel doping concentration
3. ✔ Reducing channel length
4. ✘ Decreasing channel doping concentration

Question Number : 55 Question Id : 6364312815 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is  
Question Mandatory : No Option Orientation : Vertical  
Correct Marks : 1 Wrong Marks : 0

If differential amplifier has differential gain of 20,000. CMRR = 80dB then  
common mode gain is

Options :

1. ✘ 1
2. ✔ 2

3. ✘ 0.5

4. ✘ 0

**Question Number : 56 Question Id : 6364312816 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

Advantage of negative feedback is

**Options :**

1. ✘ Decreased bandwidth

2. ✔ Increased stability

3. ✘ Reduction in gain

4. ✘ Higher output impedance

**Question Number : 57 Question Id : 6364312817 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

A two-stage amplifier with negative feedback has an overshoot when damping factor  $K$  is

**Options :**

1. ✘ Negative
2. ✘ Positive
3. ✔ Less than unity
4. ✘ Greater than unity

**Question Number : 58 Question Id : 6364312818 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

Silicon diode is less suited for low voltage rectifier operation because

**Options :**

1. ✔ Its cut-in voltage is high
2. ✘ It cannot withstand with high temperature
3. ✘ Its breakdown voltage is high
4. ✘ Its reverse saturation current is low

**Question Number : 59 Question Id : 6364312819 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

Correct Marks : 1 Wrong Marks : 0

Which of the following power amplifier has maximum efficiency

Options :

1. ✘ Class B
2. ✘ Class AB
3. ✔ Class C
4. ✘ Class A

Question Number : 60 Question Id : 6364312820 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

What is the drain current for a D-MOSFET having the characteristics values of  $I_{DSS}$  10 mA,  $V_{GS(off)}$  of -4V and  $V_{GS}$  of +2V

Options :

1. ✘ 18.5 mA
2. ✘ 5.0mA
3. ✔ 22.5mA
4. ✘ 2.25mA

Question Number : 61 Question Id : 6364312821 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

A Hartley oscillator is used for generating

Options :

1. ✘ Microwave oscillation
2. ✘ Very low frequency oscillation
3. ✔ Radio-frequency oscillation
4. ✘ Audio frequency oscillation

Question Number : 62 Question Id : 6364312822 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The maximum power dissipation capacity of a transistor is 50 mW. If the collector emitter voltage is 10 V. What is the safe collector current that can be allowed through the transistors

Options :

1. ✘ 2mA



- 2. ✘ 1mA
- 3. ✘ 2.5 mA
- 4. ✔ 5 mA

**Question Number : 63 Question Id : 6364312823 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

An operational-amplifier possesses

**Options :**

- 1. ✘ Very small input resistance and very large output resistance
- 2. ✘ Very large input resistance and very large output resistance
- 3. ✘ Very small input resistance and very small output resistance
- 4. ✔ Very large input resistance and very small output resistance

**Question Number : 64 Question Id : 6364312824 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

An RC amplifier stage has bandwidth of 500 KHz. What will be the rise time of the amplifier stage

Options :

1. ✘ 0.35ms
2. ✘ 0.1ms
3. ✔ 0.7  $\mu$ s
4. ✘ 2.0  $\mu$ s

Question Number : 65 Question Id : 6364312825 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

An amplifier will generate stable sinusoidal oscillations if we provide feedback such that

Options :

1. ✘ Its poles lie on the negative real axis in the s-plane
2. ✘ Its poles lie anywhere in the s-plane
3. ✔ Its poles lie close to  $j\omega$ -axis in the right half of s-plane

4. ✘ Its poles lie close to  $j\omega$ -axis in the left half of s-plane

Question Number : 66 Question Id : 6364312826 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

If  $X=1$  in the logic equation  $[X+Z\{\bar{Y} + (\bar{Z} + X\bar{Y})\}] \{\bar{X} + \bar{Z}(X+Y)\}=1$ . Then

Options :

- 1. ✘  $Y = Z$
- 2. ✘  $Y = \bar{Z}$
- 3. ✘  $Z = 1$
- 4. ✔  $Z = 0$

Question Number : 67 Question Id : 6364312827 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

$X = 01110$  and  $Y = 11001$  are two 5-bit binary numbers represented in two's complement format. The sum of  $X$  and  $Y$  represented in two's complement format using 6 bits is

Options :

- 1. ✘ 100111

2. ✘ 001000

3. ✔ 000111

4. ✘ 101001

**Question Number : 68 Question Id : 6364312828 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The Boolean function  $Y = AB + CD$  is to be realized using only 2-input NAND gates. The minimum number of gates required is

**Options :**

1. ✘ 2

2. ✔ 3

3. ✘ 4

4. ✘ 5

**Question Number : 69 Question Id : 6364312829 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

A new Binary Coded Pentary (BCP) number system is proposed in which every digit of a base-5 number is represented by its corresponding 3-bit binary code. For example, the base-5 number 24 will be represented by its BCP code 010100. In this numbering system, the BCP code 100010011001 corresponds to the following number in base-5 system

Options :

1. ✘ 423
2. ✘ 1324
3. ✘ 2201
4. ✔ 4231

Question Number : 70 Question Id : 6364312830 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The minimum number of 2 to 1 multiplexers required to realize a 4 to 1 multiplexers is

Options :

1. ✘ 1
2. ✘ 2

3. ✓ 3

4. ✗ 4

**Question Number : 71 Question Id : 6364312831 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

11001, 1001 and 111001 correspond to the 2's complement representation of which one of the following sets of number

**Options :**

1. ✗ 25, 9 and 57 respectively

2. ✗ -6, -6 and -6 respectively

3. ✓ -7, -7 and -7 respectively

4. ✗ -25, -9 and -57 respectively

**Question Number : 72 Question Id : 6364312832 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

A 0 to 6 counter consists of 3 flip flops and a combination of 2 input gate(s). The combination circuit consists of

**Options :**

1. ✘ One AND gate
2. ✘ One OR gate
3. ✘ One AND gate and one OR gate
4. ✔ Two AND gates

**Question Number : 73 Question Id : 6364312833 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The output of the 74 series of TTL gates is taken from a BJT in

**Options :**

1. ✘ Totem pole and common collector configuration
2. ✔ Either totem pole or open collector configuration
3. ✘ Common base configuration
4. ✘ Common collector configuration

**Question Number : 74 Question Id : 6364312834 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

Correct Marks : 1 Wrong Marks : 0

After executing the below code, contents of Accumulator (A) and Z, AC, CY flag bits are \_\_\_\_\_

```
MIV A, F9H
ANI 83 H
```

Options :

1. ✓ A = 81H, Z = 0, AC = 0, CY = 0
2. ✗ A = F3H, Z = 1, AC = 0, CY = 1
3. ✗ A = F9H, Z = 1, AC = 0, CY = 0
4. ✗ A = 83H, Z = 0, AC = 0, CY = 0

Question Number : 75 Question Id : 6364312835 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

A digital system is required to amplify a binary-encoded audio signal. The user should be able to control the gain of the amplifier from a minimum to a maximum in 100 increments. The minimum number of bits required to encode, in straight binary is

Options :

1. ✗ 8



2. ✘ 6

3. ✘ 5

4. ✔ 7

**Question Number : 76 Question Id : 6364312836 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The Boolean expression  $AC+B\bar{C}$  is equivalent to

**Options :**

1. ✘  $\bar{A}C+B\bar{C}+AC$

2. ✘  $\bar{B}C + AC + B\bar{C}+\bar{A}C\bar{B}$

3. ✘  $AC + B\bar{C}+\bar{B}C + ABC$

4. ✔  $ABC + AB\bar{C} + \bar{A}B\bar{C}+A\bar{B}C$

**Question Number : 77 Question Id : 6364312837 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

Two D flip-flops are connected as a synchronous counter that goes through the following  $Q_B, Q_A$  sequence

$00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \rightarrow \dots$

The combination to the inputs  $D_A$  and  $D_B$  are

Options :

1. ✘  $D_A = Q_B; D_B = Q_A$

2. ✘  $D_A = \bar{Q}_A; D_B = \bar{Q}_B$

3. ✘  $D_A = (Q_A \bar{Q}_B + Q_B \bar{Q}_A); D_B = \bar{Q}_A$

4. ✔  $D_A = (Q_A Q_B + \bar{Q}_A \bar{Q}_B); D_B = \bar{Q}_B$

Question Number : 78 Question Id : 6364312838 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The range of the signed decimal numbers that can be represented by 6-bit 1's complement number is

Options :

1. ✔ -31 to +31

2. ✘ -63 to +64

3. ✘ -64 to +63

4. ✘ -32 to +31

**Question Number : 79 Question Id : 6364312839 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

When a human being tries to approach an object, his brain acts as

**Options :**

1. ✘ An actuator

2. ✔ A controller

3. ✘ An amplifier

4. ✘ An error measuring device

**Question Number : 80 Question Id : 6364312840 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The impulse response of a linear time invariant system is given as

$$g(t) = e^{-t}, t > 0$$

The transfer function of the system is equal to

Options :

1. ✘  $\frac{S}{(S+1)}$

2. ✘  $\frac{1}{S(S+1)}$

3. ✔  $\frac{1}{(S+1)}$

4. ✘  $\frac{1}{S}$

Question Number : 81 Question Id : 6364312841 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

If the characteristics equation of a closed loop system is  $2S^2 + 6S + 6 = 0$  then system is

Options :

1. ✘ Undamped

2. ✓ Underdamped
3. ✗ Overdamped
4. ✗ Critically damped

Question Number : 82 Question Id : 6364312842 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

Given a unity feedback system  $G(S) = \frac{K}{S(S+4)}$ . What is the value of K for a damping ratio of 0.5

Options :

1. ✗ 2
2. ✗ 4
3. ✓ 16
4. ✗ 1

Question Number : 83 Question Id : 6364312843 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

A system has single pole at origin, its impulse response will be

Options :

1. ✘ Ramp
2. ✘ Oscillatory
3. ✔ Constant
4. ✘ Decaying exponential

Question Number : 84 Question Id : 6364312844 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The feedback system with the characteristics equation  $s^4 + 20Ks^3 + 5s^2 + 10s + 15 = 0$ , system is

Options :

1. ✘ Stable for non-zero value of K
2. ✘ Stable for all value of K
3. ✔ Unstable for all value of K
4. ✘ Stable for  $\infty > K > 7$

Question Number : 85 Question Id : 6364312845 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

If the gain of open loop system is doubled then the gain margin of the system is

Options :

1. ✓ Halved
2. ✗ Doubled
3. ✗ Not effected
4. ✗ One fourth of original value

Question Number : 86 Question Id : 6364312846 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

In the root-locus for open loop transfer function

$$G(S)H(S) = \frac{K(S+6)}{(S+3)(S+5)}$$

The break away points are located respectively at

Options :

1. ✗ 2

2. ✘ -4.27

3. ✘ 1

4. ✔ -7.73

**Question Number : 87 Question Id : 6364312847 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The frequency where magnitude M has a peak value in frequency response is

Options :

1. ✘ Tuned frequency

2. ✔ Resonant Frequency

3. ✘ Peak frequency

4. ✘ Normalized frequency

**Question Number : 88 Question Id : 6364312848 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**



Considered the following open loop transfer function

$$G(S) = \frac{K(S+2)}{(S+1)(S+4)}$$

Characteristics equation of the unity negative feedback will be

Options :

1. ✘  $S^2 + 5S + 14 + K(S + 2) = 0$

2. ✘  $S^2 + 10S + 4 + K(S + 1) = 0$

3. ✘  $S^2 + 10S - 4 + K(S + 2) = 0$

4. ✔  $S^2 + 5S + 4 + K(S + 2) = 0$

Question Number : 89 Question Id : 6364312849 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The attenuation (magnitude) by a lead compensator at a frequency of maximum

phase lead  $\omega_m = \sqrt{ab}$  is

Options :

1. ✘  $\sqrt{a + b}$

2. ✘  $\sqrt{b-a}$

3. ✔  $\sqrt{\frac{a}{b}}$

4. ✘  $\sqrt{\frac{b}{a}}$

Question Number : 90 Question Id : 6364312850 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

A unity-feedback control system has open loop transfer function

$$G(S) = \frac{4(2S+1)}{S^2(S+2)}$$

If the input to the system is unit ramp, then steady state error will be

Options :

1. ✘ 5

2. ✔ 0

3. ✘ 2

4. ✘ Infinite

Question Number : 91 Question Id : 6364312851 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

Which of the following statement is correct

Options :

1. ✘ Phase margin is always negative for stable system
2. ✔ Phase margin is always positive for stable system
3. ✘ Phase margin can be negative or positive for stable system
4. ✘ Phase margin is always zero for stable system

Question Number : 92 Question Id : 6364312852 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The state space representation of a linear time invariant system is

$$X(t) = AX(t) + Bu(t); \quad Y(t) = CX(t);$$

What is the transfer function  $H(s)$  of the system

Options :

1. ✓  $C(sI - A)^{-1}B$

2. ✗  $B(sI - A)^{-1}C$

3. ✗  $C(sI - A)B$

4. ✗  $B(sI - A)C$

Question Number : 93 Question Id : 6364312853 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

Open loop transfer function of a system having one zero with positive real value is

Options :

1. ✗ Positive phase function

2. ✓ Non-minimum phase function

3. ✗ Negative phase function

4. ✗ Zero phase function

Question Number : 94 Question Id : 6364312854 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

**Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

The modulation index of an AM wave is changed from 0 to 1. Transmitted power is

**Options :**

1. ✘ Halved
2. ✘ Quadrupled
3. ✘ Unchanged
4. ✔ Increased by 50 %

**Question Number : 95 Question Id : 6364312855 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is**

**Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

A linear system has the transfer function

$$H(j) = \frac{1}{(j\omega+1)}$$

When it is subjected to an input white noise process with a constant spectral density 'A', the spectral density of the output will be

**Options :**

1. ✘  $\frac{1}{(j\omega+1)}$

2. ✘ 
$$\frac{A}{(j\omega+1)^2}$$

3. ✔ 
$$\frac{A}{(\omega^2+1)}$$

4. ✘ 
$$\frac{A}{\sqrt{(\omega^2+1)}}$$

**Question Number : 96 Question Id : 6364312856 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

An antenna has 40 ohm antenna resistance and 60 ohm radiation resistance. The efficiency of the antenna is

**Options :**

1. ✔ 60 %

2. ✘ 80%

3. ✘ 20%

4. ✘ 40%

Question Number : 97 Question Id : 6364312857 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

A communication channel with AWGN operating at a signal to noise ratio  $SNR \gg 1$  and bandwidth  $B$  has capacity  $C_1$ . If the SNR is doubled keeping  $B$  constant. The resultant capacity  $C_2$  is

Options :

1. ✘  $C_2 = 2 C_1$
2. ✘  $C_2 = C_1 + 2B$
3. ✘  $C_2 = C_1 + 0.3B$
4. ✔  $C_2 = C_1 + B$

Question Number : 98 Question Id : 6364312858 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

If  $E$  denotes expectation, the variance of a random variable  $X$  is given as

Options :

1. ✘  $E[X^2] + E^2[X]$

2. ✓  $E[X^2] - E^2[X]$

3. ✗  $E^2[X]$

4. ✗  $E[X^2]$

Question Number : 99 Question Id : 6364312859 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

Which of the following analog modulation scheme required minimum transmitted power and minimum bandwidth

Options :

1. ✗ Amplitude Modulation

2. ✓ SSB

3. ✗ DSB-SC

4. ✗ DSB-FC

Question Number : 100 Question Id : 6364312860 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0



The random variable

$$Y = \int_{-\infty}^{\infty} W(t)\phi(t)dt$$

$$\text{Where } \phi(t) = \begin{cases} 1; & 5 \leq t \leq 7 \\ 0; & \text{otherwise} \end{cases}$$

and  $W(t)$  is a real white Gaussian noise process with two-sided power spectral density  $S_{W(f)}=3\text{W/Hz}$ , for all  $f$ . The variance of  $Y$  is

Options :

1. ✘ 2

2. ✔ 6

3. ✘ 7

4. ✘ 9

Question Number : 101 Question Id : 6364312861 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

A single bit, equally likely to be 1 and 0, is to be sent across an AWGN channel with PSD  $N_0/2$ . Binary signaling, with 0 for  $P(t)$  and 1 for  $q(t)$ , is used for transmission, along with an optimal receiver that minimizes the bit error probability.

Let  $\psi_1(t)$ ,  $\psi_2(t)$ , form an orthogonal signal set.

If we choose  $P(t) = \psi_1(t)$ , and  $q(t) = -\psi_1(t)$  we would obtain a certain bit-error probability  $P_b$ .

If we keep  $P(t) = \psi_1(t)$  but take  $q(t) = \sqrt{E} \psi_2(t)$ , for what value of  $E$  would we obtain the same bit-error probability  $P_b$

Options :

1. ✘ 1
2. ✘ 0
3. ✘ 2
4. ✔ 3

Question Number : 102 Question Id : 6364312862 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

Let  $(X_1$  and  $X_2)$  be independent random variables.  $X_1$  has mean 0 and variance 1, while  $X_2$  has mean 1 and variance 4. The mutual information  $I(X_1; X_2)$  between  $X_1$  and  $X_2$  in bits is

Options :

1. ✘ 1

2. ✘ 4

3. ✔ 0

4. ✘ 6

**Question Number : 103 Question Id : 6364312863 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

The channel capacity under the gaussian noise for a discrete memory less channel with bandwidth of 4 MHz and SNR of 31 is

**Options :**

1. ✘ 4 Kbps

2. ✘ 2Kbps

3. ✘ 4Mbps

4. ✔ 20Mbps

**Question Number : 104 Question Id : 6364312864 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

Correct Marks : 1 Wrong Marks : 0

A binary random variable X takes the value +2 and -2. The probability  $P(X = +2) = a$ .

The value of a, for which the entropy of X is maximum

Options :

1. ✓ 0.5

2. ✗ 1

3. ✗ 2

4. ✗ 4

Question Number : 105 Question Id : 6364312865 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The bandwidth required in DPCM is less than that of PCM because

Options :

1. ✗ More quantization levels are needed

2. ✗ The difference signal is larger in amplitude than actual signal

3. ✓ The no. of bits per code is reduced resulting in a reduced bit rate

4. ✘ The successive samples of signal often differ in amplitude

Question Number : 106 Question Id : 6364312866 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

An analog signal is sampled at 36 KHz and quantized in to 256 levels. The time duration of a bit of the binary coded signal is

Options :

- 1. ✘ 5.43ms
- 2. ✔ 3.47 $\mu$ s
- 3. ✘ 6.47  $\mu$ s
- 4. ✘ 1.47ms

Question Number : 107 Question Id : 6364312867 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

A source delivers symbols A, B, C, D with probabilities  $1/2$ ,  $1/4$ ,  $1/8$  and  $1/8$ . Entropy of the system is

Options :

- 1. ✔ 1.75 bits per symbol

- 2. ✘ 1.75 bits per second
- 3. ✘ 1.25 symbols per bit
- 4. ✘ 1.75 symbols per second

Question Number : 108 Question Id : 6364312868 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The expression for an electric field in free space is  $E = E_0 = (x + y + j2z)e^{-j(\omega t - kx + ky)}$  where  $x, y, z$  represents the spatial coordinates,  $t$  represents time, and  $\omega, k$  are constants. This electric field

Options :

- 1. ✘ Represents a linearly polarized plane wave
- 2. ✘ Does not represent a plane wave
- 3. ✔ Represents an elliptically polarized plane wave propagating along x-y plane
- 4. ✘ Represents a circular polarized plane wave propagating normal to the z-axis

Question Number : 109 Question Id : 6364312869 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is

**Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

Radiation resistance of a small dipole current element of length  $l$  at a frequency of 3 GHz is 3 ohms. If the length is changed by 1%, then the percentage change in the radiation resistance,

**Options :**

1. ✘ 3%

2. ✘ 4%

3. ✔ 2%

4. ✘ No change

**Question Number : 110 Question Id : 6364312870 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical**

**Correct Marks : 1 Wrong Marks : 0**

For a vector field  $A$  which one of the following is false

**Options :**

1. ✔ A is irrotational if  $\nabla^2 \times A = 0$

2. ✘  $\nabla \times A$  in another vector field

3. ✘ A is sinusoidal if  $\nabla \cdot A = 0$

4. ✘  $\nabla \times (\nabla \times A) = \nabla (\nabla \cdot A) - \nabla^2 A$

**Question Number : 111 Question Id : 6364312871 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

Solutions of Laplace's equation, which are continuous through the second derivative are called

Options :

1. ✘ Odd functions
2. ✘ Fundamental functions
3. ✘ Bessel functions
4. ✔ Harmonic functions

**Question Number : 112 Question Id : 6364312872 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

For electromagnetic wave propagation in free space, the free space is defined as

Options :

1. ✘  $\sigma = 0; \varepsilon = 1; \mu \neq 1; \rho = 0; J = 0$



2. ✘  $\sigma \neq 0; \varepsilon > 1; \mu < 1; p \neq 0; J = 0$

3. ✔  $\sigma = 0; \varepsilon = 1; \mu = 1; p = 0; J = 0$

4. ✘  $\sigma = 0; \varepsilon = 1; \mu = 1; p \neq 0; J \neq 0$

Question Number : 113 Question Id : 6364312873 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

Which of the following statement is correct.

On a conducting surface boundary, electric field lines are

Options :

1. ✔ Always normal

2. ✘ Always tangential

3. ✘ At an angle depending on the field intensity

4. ✘ Neither normal nor tangential

Question Number : 114 Question Id : 6364312874 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

In a field of charge  $Q$  at the origin, the potentials at  $A(2,0,0)$  and  $B(1/2,0,0)$  are  $V_A=15$  volt and  $V_B=0$  volt respectively. What will be the potential at  $C(1,0,0)$

Options :

1. ✓ 20volt
2. ✗ 22volt
3. ✗ 17volt
4. ✗ 18volt

Question Number : 115 Question Id : 6364312875 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical

Correct Marks : 1 Wrong Marks : 0

The value of  $\nabla \cdot A$ , where  $A=3XYa_x+Xa_y+XYa_z$  at a point  $(2, -2, 2)$  is

Options :

1. ✗ 4
2. ✗ 5
3. ✗ -6
4. ✓ -10

Question Number : 116 Question Id : 6364312876 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

In a uniform plane wave, the value of  $|E|/|H|$  is

Options :

1

1. ✘

$$\sqrt{\frac{\mu}{\epsilon}}$$

2. ✔

$$\sqrt{\mu\epsilon}$$

3. ✘

$$\sqrt{\frac{\epsilon}{\mu}}$$

4. ✘

Question Number : 117 Question Id : 6364312877 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

Poynting vector is a measure of which of the following

Options :

1. ✓ Average power flow through the surface
2. ✘ Power dissipated by the surface
3. ✘ Maximum power flow through a surface surrounding the source
4. ✘ Instantaneous power flow through the surface

**Question Number : 118 Question Id : 6364312878 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0**

A uniform transmission line of characteristics impedance 100 ohm and feeding a purely resistive load of 500 ohm uses single stub matching. The stub is placed at a distance  $d$  from the load. The VSWR on the length  $d$  will be

**Options :**

1. ✘ 1
2. ✘ 0
3. ✓ 5
4. ✘ 4

Question Number : 119 Question Id : 6364312879 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

The cut off wavelength  $\lambda_c$  for TE<sub>20</sub> mode for a standard rectangular waveguide is

Options :

1. ✘ 2a

2. ✘ 2/a

3. ✘ 3a

4. ✔ a

Question Number : 120 Question Id : 6364312880 Question Type : MCQ Option Shuffling : Yes Display Question Number : Yes Is Question Mandatory : No Option Orientation : Vertical Correct Marks : 1 Wrong Marks : 0

Which of the following antenna is obtained by modifying a wave guide'

Options :

1. ✘ Helical antenna

2. ✔ Horn antenna

3. ✘ Dipole antenna

#### 4. ✖ Microstrip antenna